



# **Subject- Physics**

## **Semester-IV**

### **Unit:- 1 Solid State Electronics**

By

**Dr. Deepak Taikar**


**Head, Dept. of Physics**

**Shri Lemdeo Patil Mahavidyalaya, Mandhal**




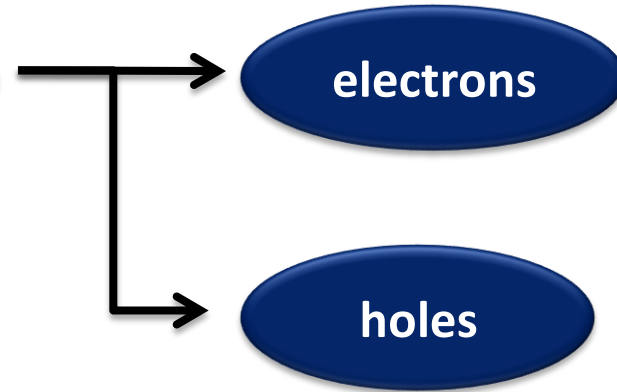
# Bipolar Junction Transistor

- ❖ Transistor = transfer + resistor
- ❖ It transfer signal from low to high resistance.
- ❖ Bipolar junction transistor (BJT)



# Types of Transistor

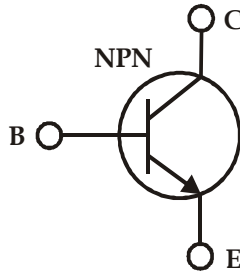
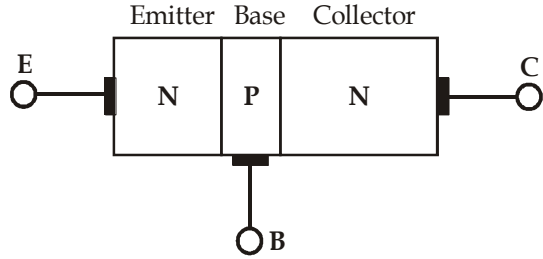


**a) Emitter:- supplies charge carriers**

(electrons or holes).

It is **heavily doped** and is always connected in forward bias with respect to base, so that it can inject large number of majority charge carrier into the base region.

It is **moderate in size**.

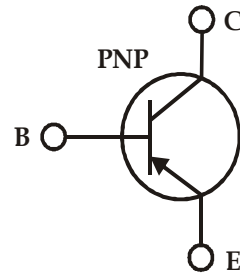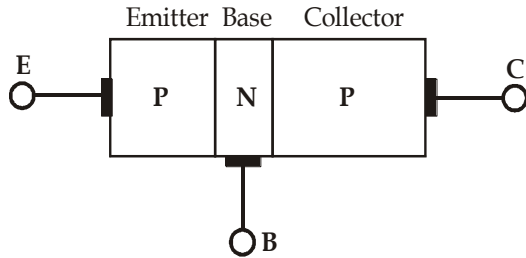


**b) Base:-** It is **lightly doped** and very **thin** so that most of the emitter injected charge carrier passed to the collector region.


**c) Collector:-** collector collects charge carrier emitted by emitter.

The collector is **moderately doped** and is **wider** than both base and emitter.

# Working of N-P-N transistor

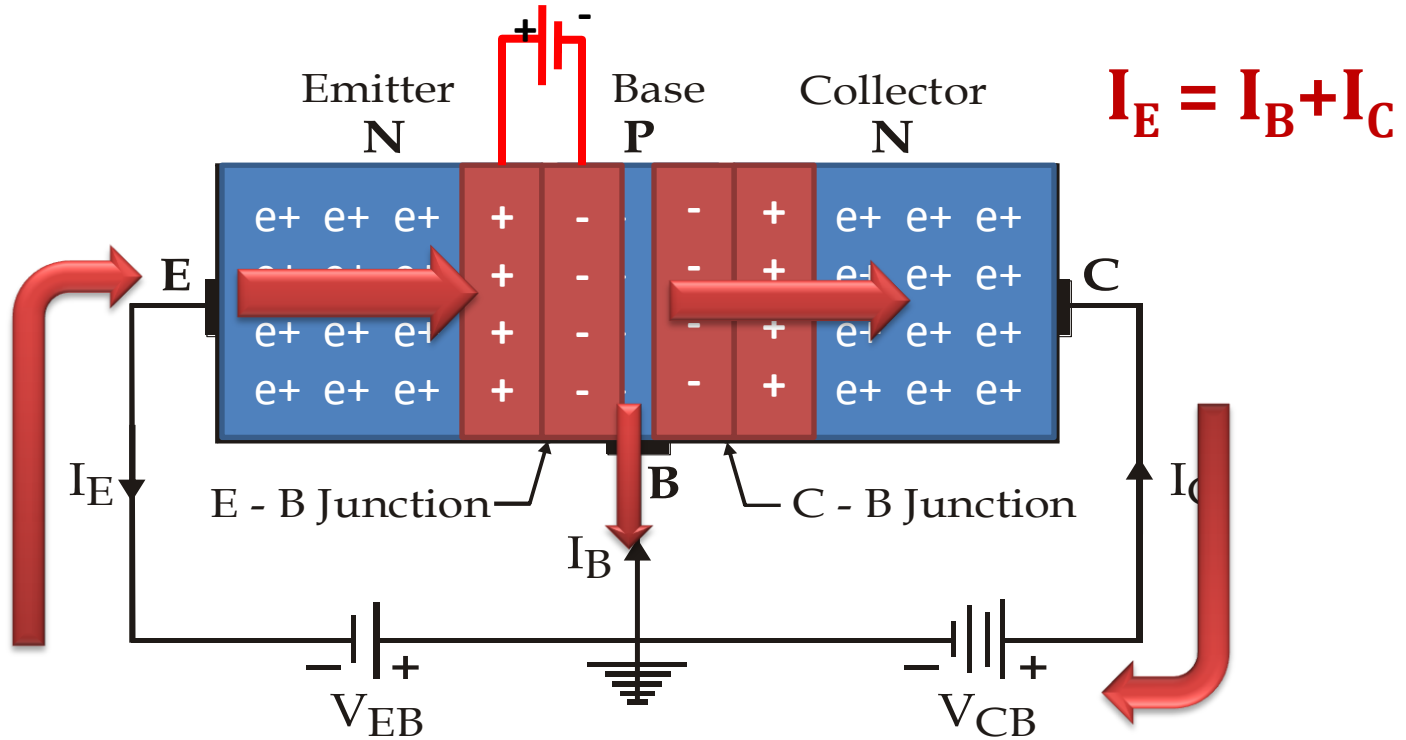

# Working of PNP transistor

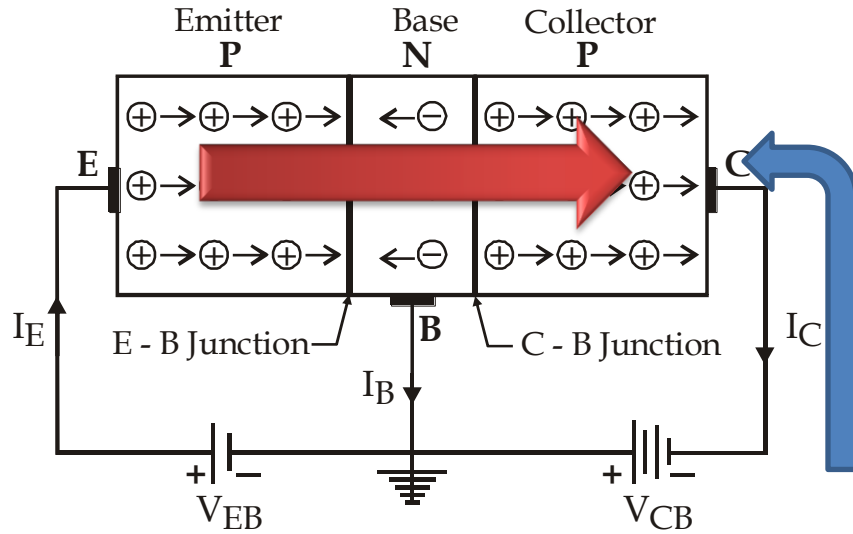



1. As hole reach collector region, a fresh electron is released from negative terminal of battery  $V_{CB}$  and recombine with holes.

2. Also for each hole which is lost in collector region, a covalent bond is broken in the emitter and electron is liberated which enters the positive terminal of  $V_{EB}$  and the holes produce move towards base



3. In PNP transistor, the current flow inside the transistor is carried by holes and in external circuit by electrons

# Transistor Configuration or Mode

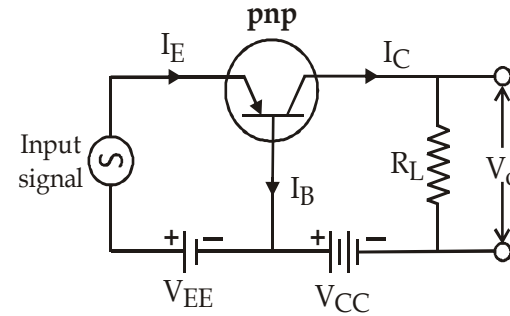
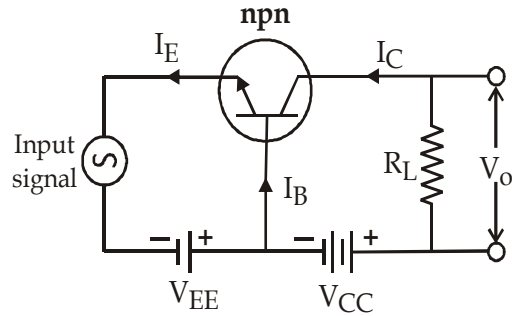
## 1) Common Base configuration (CB mode):



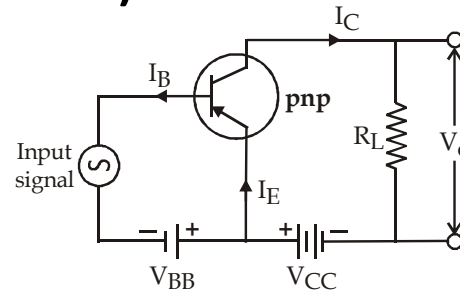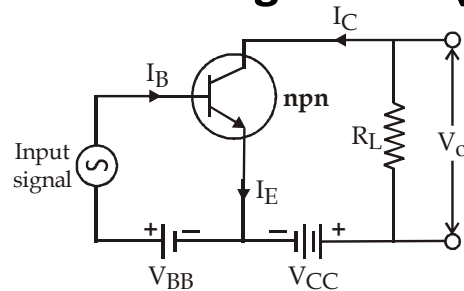
## 2) Common Emitter configuration (CE mode):



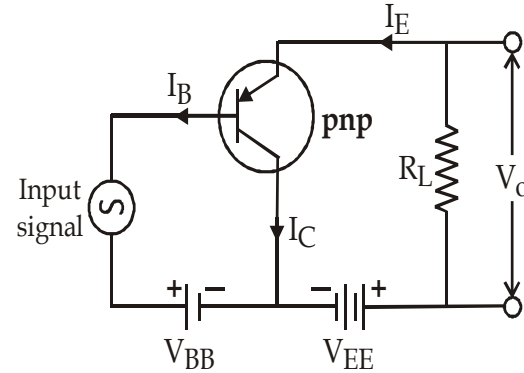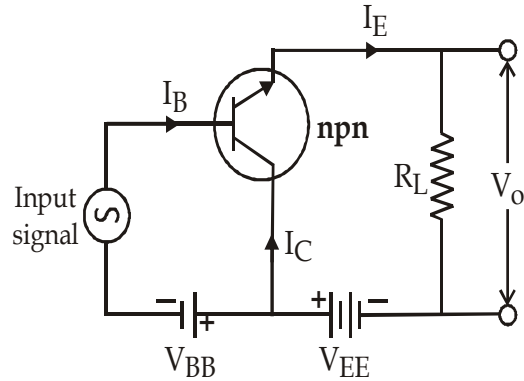- **3) Common Collector configuration (CC mode):**



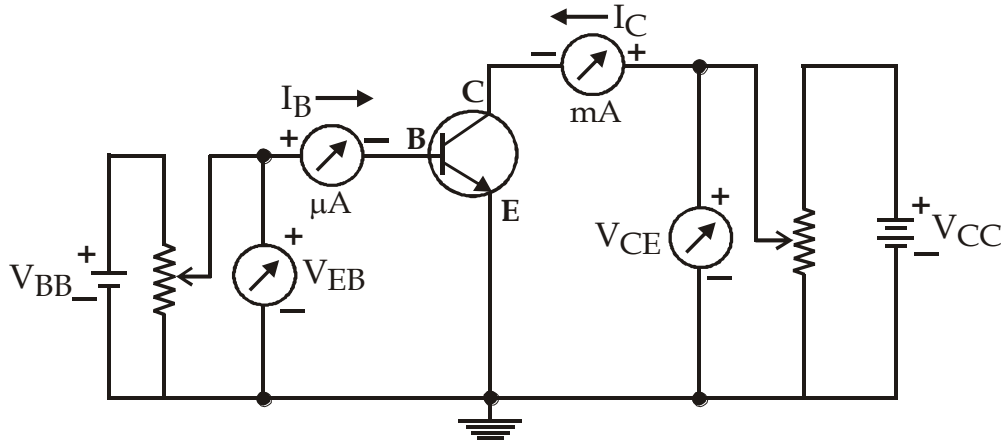
# Characteristic of NPN transistor in CE mode




$$r_i = \left( \frac{\Delta V_{BE}}{\Delta I_B} \right)$$

## Input Characteristic

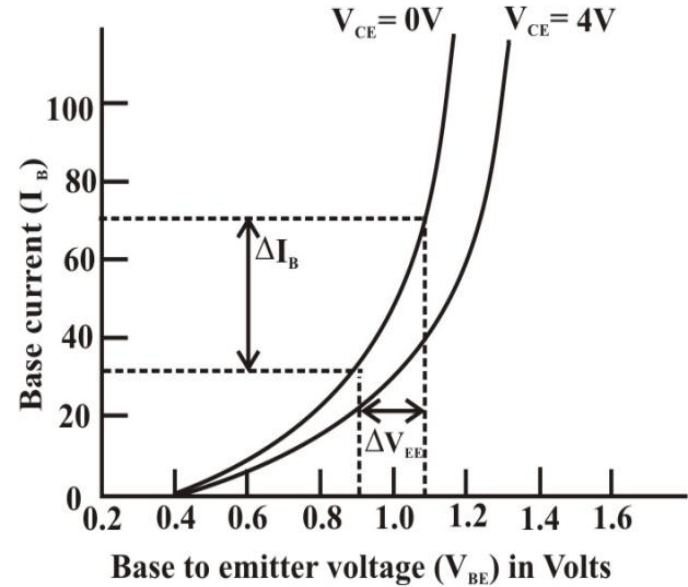



# Out put characteristic

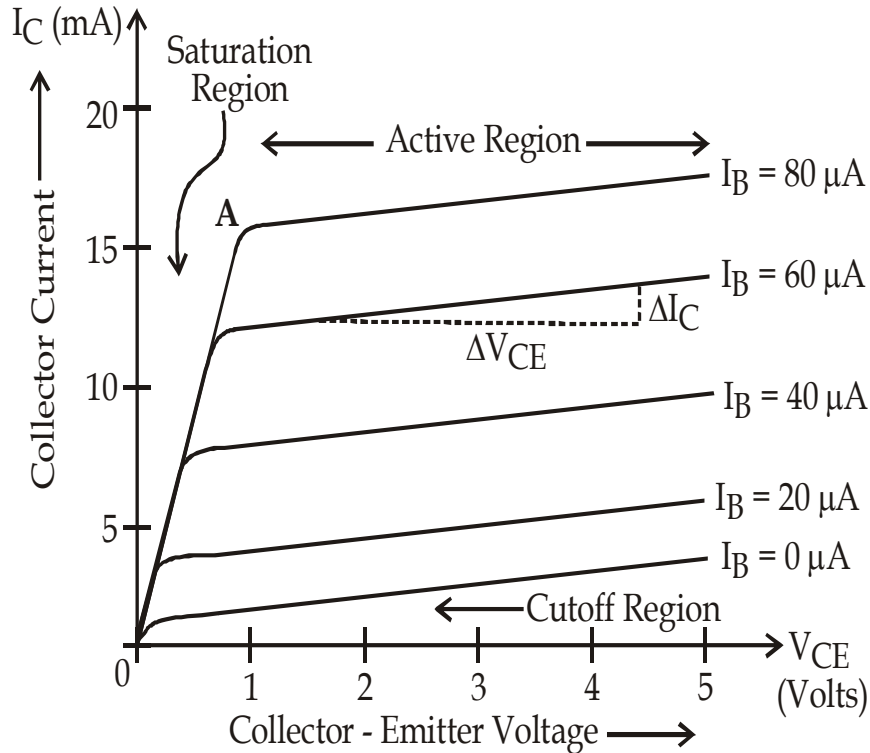


**a) Saturation Region:** The region of the curve to the left of the line OA is known as saturation region. In this region both junctions are forward biased.

**b) Cut-off Region:** The region below the curve  $I_B=0$  is known as cut-off region. In this region both the junction are reversed biased.

**c) Active Region:** The central region where the curve are uniform in spacing is called as active region. In this region E-B junction is forward biased and C-B junction is reversed biased.


$$\beta = \left( \frac{\Delta I_C}{\Delta I_B} \right)$$

# Transfer characteristic

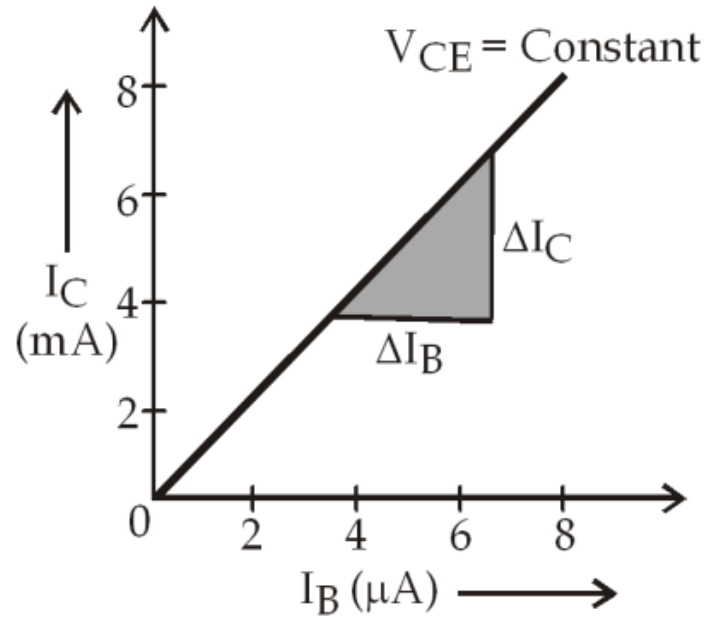


$$\beta = \left( \frac{\Delta I_C}{\Delta I_B} \right)$$
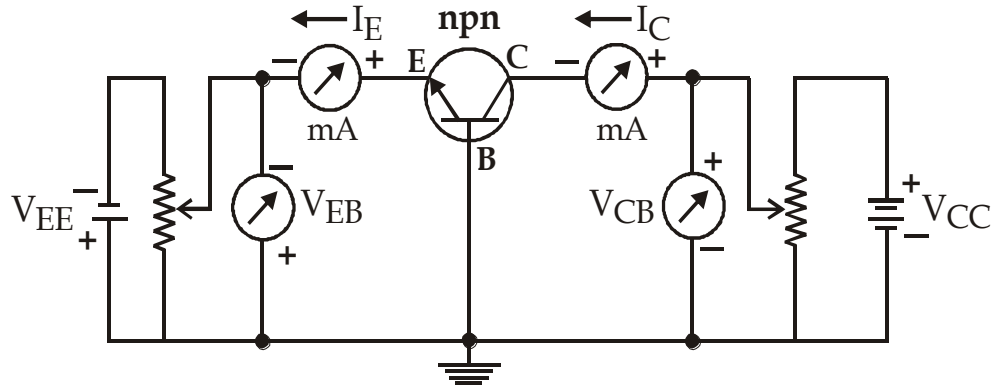
# Characteristic of NPN transistor in CB mode




## Input Characteristic

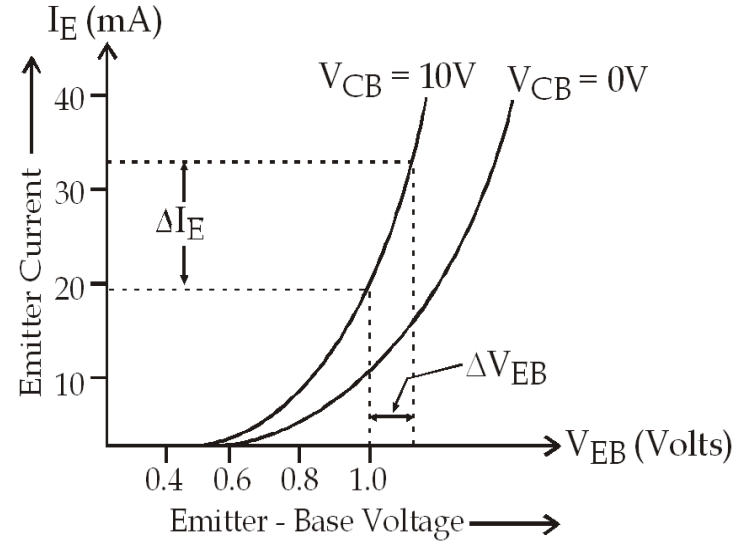


$$r_i = \left( \frac{\Delta V_{EB}}{\Delta I_E} \right)$$

# Out put characteristic

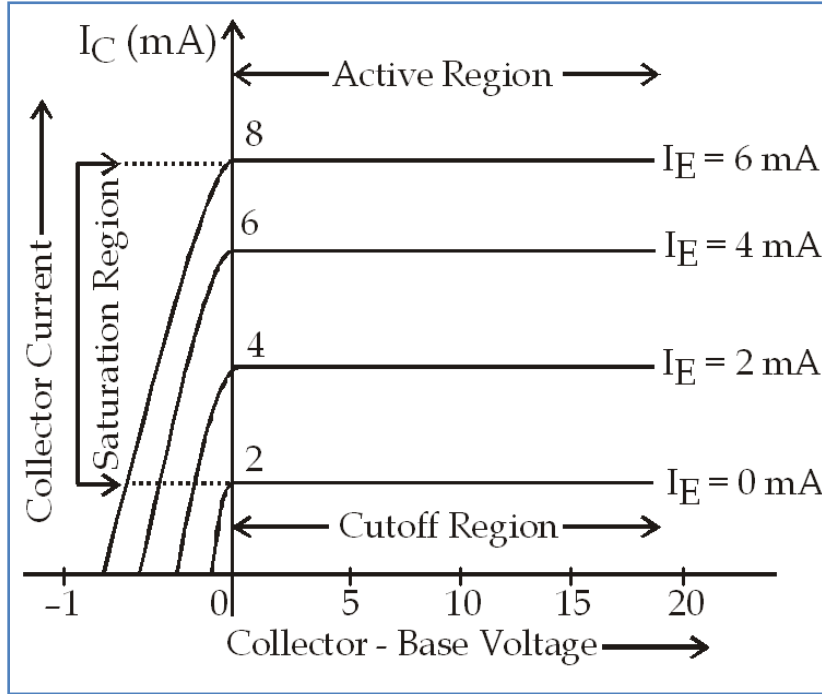

# Transfer characteristic

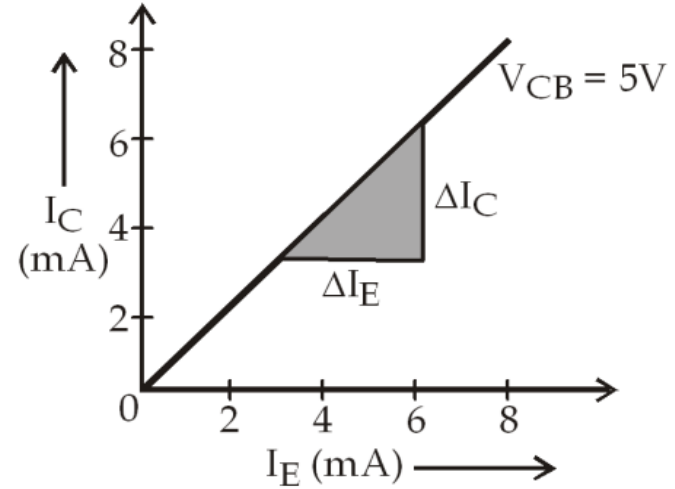

$$\alpha = \left( \frac{\Delta I_C}{\Delta I_E} \right)$$

# Relation between $\alpha$ and $\beta$

The emitter current in the circuit is given by,  $I_E = I_B + I_C$

For small change, we have,  $\Delta I_E = \Delta I_B + \Delta I_C$

Divide by  $\Delta I_C$ , we get,  $\frac{\Delta I_E}{\Delta I_C} = \frac{\Delta I_B}{\Delta I_C} + 1$

But,  $\alpha = \left(\frac{\Delta I_C}{\Delta I_E}\right)$  and  $\beta = \left(\frac{\Delta I_C}{\Delta I_B}\right)$

$$\therefore \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\therefore \frac{1}{\alpha} = \frac{1+\beta}{\beta}$$

$$\therefore \alpha = \left(\frac{\beta}{1+\beta}\right)$$

And,  $\frac{1}{\beta} = \frac{1}{\alpha} - 1$

$$\therefore \frac{1}{\beta} = \frac{1-\alpha}{\alpha}$$

$$\therefore \beta = \left(\frac{\alpha}{1-\alpha}\right)$$